

FIGURE 7-8 Simulation results for *Binary_Counter_Part_RTL_by_3* with a control unit to increment the datapath counter every third cycle.

 


FIGURE 7-9 Circuit synthesized for *Control_Unit_by_3*, the control unit of *Binary_Counter_Part_RTL_by_3*, a 4-bit binary counter partitioned into a control unit and a datapath unit, with the counter incrementing every third clock cycle.

7.3 Design and Synthesis of a RISC Stored-Program Machine

RISCs are designed to have a small set of instructions that execute in short clock cycles, with a small number of cycles per instruction. RISC machines are optimized to achieve efficient pipelining of their instruction streams [2]. In this section, we will model a simple RISC machine. Our companion Web site (www.pearsonhighered.com/ciletti) includes the machine's source code and an assembler that can be used to develop programs for student projects. The machine also serves as a starting point for developing architectural variants and a more robust instruction set.

Designers make high-level trade-offs in selecting an architecture that serves an application. Once an architecture has been selected, a circuit that has sufficient performance (speed) must be synthesized to implement the machine. Hardware description languages (HDLs) play a key role in this process by modeling the system and serving as a descriptive medium that can be used by a synthesis tool.

As an example, the overall architecture of a simple RISC is shown in Figure 7-10. *RISC_SPM* is a stored-program RISC-architecture machine [3, 4]—its instructions are contained in a program stored in memory.

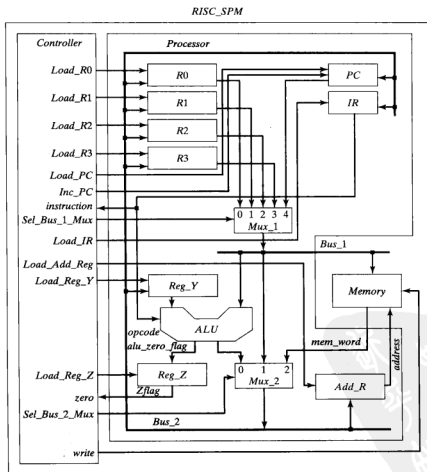


FIGURE 7-10 Architecture of *RISC_SPM*, an RISC stored-program machine (SPM).

The machine consists of three functional units: a processor (datapath unit), a controller (control unit), and memory. Program instructions and data are stored in memory. In program-directed operation, instructions are fetched synchronously from memory, decoded, and executed to (1) operate on data within the arithmetic and logic unit (*ALU*), (2) change the contents of storage registers, (3) change the contents of the program counter (*PC*), instruction register (*IR*), and the address register (*ADD_R*), (4) change the contents of memory, (5) retrieve data and instructions from memory, and (6) control the movement of data on the system busses. The instruction register contains the instruction that is currently being executed; the program counter contains the address of the next instruction to be executed; and the address register holds the address of the memory location that will be addressed next by a read or write operation.

7.3.1 RISC SPM: Processor

The processor includes registers, datapaths, control signals, and an *ALU* capable of performing arithmetic and logic operations on its operands, subject to the opcode held in the instruction register. A multiplexer, *Mux_1*, determines the source of data that is bound for *Bus_1*, and a second mux, *Mux_2*, determines the source of data bound for *Bus_2*. The input datapaths to *Mux_1* are from four internal general-purpose registers (*R0*, *R1*, *R2*, *R3*), and from the *PC*. The contents of *Bus_1* can be steered to the *ALU*, to memory, or to *Bus_2* (via *Mux_2*). The input datapaths to *Mux_2* are from the *ALU*, *Mux_1*, and the memory unit. Thus, an instruction can be fetched from memory, placed on *Bus_2*, and loaded into the instruction register. A word of data can be fetched from memory and steered to a general-purpose register or to the operand register (*Reg_Y*) prior to an operation of the *ALU*. The result of an *ALU* operation can be placed on *Bus_2*, loaded into a register, and subsequently transferred to memory. A dedicated register (*Reg_Z*) holds a flag indicating that the result of an *ALU* operation is 0.⁹

7.3.2 RISC SPM: ALU

For the purposes of this example, the *ALU* has two operand datapaths, *data_1* and *data_2*, and its instruction set is limited to the following instructions:

Instruction	Action
<i>ADD</i>	Adds the datapaths to form <i>data_1 + data_2</i>
<i>SUB</i>	Subtracts the datapaths to form <i>data_1 - data_2</i>
<i>AND</i>	Takes the bitwise-and of the datapaths, <i>data_1 & data_2</i>
<i>NOT</i>	Takes the bitwise Boolean complement of <i>data_1</i>

7.3.3 RISC SPM: Controller

The timing of all activity in the machine is determined by the controller. The controller must steer data to the proper destination, according to the instruction being executed. Thus, the design of the controller is strongly dependent on the specification of the

⁹This can be used to monitor a loop index.

machine's ALU and datapath resources and the clocking scheme available. In this example, a single clock will be used, and execution of an instruction is initiated on a single edge of the clock (e.g., the rising edge). The controller monitors the state of the processing unit and the instruction to be executed and determines the value of the control signals. The controller's input signals are the instruction word and the zero flag from the ALU. The signals produced by the controller are identified as follows:

<u>Control Signal</u>	<u>Action</u>
<i>Load_Add_Reg</i>	Loads the address register
<i>Load_PC</i>	Loads <i>Bus_2</i> to the program counter
<i>Load_IR</i>	Loads <i>Bus_2</i> to the instruction register
<i>Inc_PC</i>	Increments the program counter
<i>Sel_Bus_1_Mux</i>	Selects among the <i>Program_Counter</i> , <i>R0</i> , <i>R1</i> , <i>R2</i> , and <i>R3</i> to drive <i>Bus_1</i>
<i>Sel_Bus_2_Mux</i>	Selects among <i>Alu_out</i> , <i>Bus_1</i> , and memory to drive <i>Bus_2</i>
<i>Load_R0</i>	Loads general-purpose register <i>R0</i>
<i>Load_R1</i>	Loads general-purpose register <i>R1</i>
<i>Load_R2</i>	Loads general-purpose register <i>R2</i>
<i>Load_R3</i>	Loads general-purpose register <i>R3</i>
<i>Load_Reg_Y</i>	Loads <i>Bus_2</i> to the register <i>Reg_Y</i>
<i>Load_Reg_Z</i>	Stores output of ALU in register <i>Reg_Z</i>
<i>write</i>	Loads <i>Bus_1</i> into the SRAM memory at the location specified by the address register

The control unit (1) determines when to load registers, (2) selects the path of data through the multiplexers, (3) determines when data should be written to memory, and (4) controls the three-state busses in the architecture.

7.3.4 RISC SPM: Instruction Set

The machine is controlled by a machine language program consisting of a set of instructions stored in memory. So, in addition to depending on the machine's architecture, the design of the controller depends on the processor's instruction set (i.e., the instructions that can be executed by a program). A machine language program consists of a stored sequence of 8-bit words (bytes). The format of an instruction of *RISC_SPM* can be long or short, depending on the operation.

Short instructions have the format shown in Figure 7-11(a). Each short instruction requires 1 byte of memory. The word has a 4-bit opcode, a 2-bit source register address, and a 2-bit destination register address. A long instruction requires 2 bytes of memory. The first word of a long instruction contains a 4-bit opcode. The remaining 4 bits of the word can be used to specify addresses of a pair of source and destination registers, depending on the instruction. The second word contains the address of the memory word that holds an operand required by the instruction. Figure 7-11(b) shows the 2-byte format of a long instruction.

 


FIGURE 7-11 Instruction format of (a) a short instruction and (b) a long instruction.

The instruction mnemonics and their actions are listed below.

Single-Byte Instruction

NOP

Action
No operation is performed; all registers retain their values. The addresses of the source and destination register are don't-cares, they have no effect.

ADD

Adds the contents of the source and destination registers and stores the result into the destination register.

AND

Forms the bitwise-and of the contents of the source and destination registers and stores the result into the destination register. Forms the bitwise complement of the content of the source register and stores the result into the destination register.

NOT

SUB

Subtracts the content of the source register from the destination register and stores the result into the destination register.

Two-Byte Instruction

RD

Action
Fetches a memory word from the location specified by the second byte and loads the result into the destination register. The source register bits are don't-cares (i.e., unused).

WR

Writes the contents of the source register to the word in memory specified by the address held in the second byte. The destination register bits are don't-cares (i.e., unused).

BR

Branches the activity flow by loading the program counter with the word at the location (address) specified by the second byte of the instruction. The source and destination bits are don't-cares (i.e., unused).

BRZ

Branches the activity flow by loading the program counter with the word at the location (address) specified by the second byte of the instruction if the zero flag register is asserted.

The *RISC_SPM* instruction set is summarized in Table 7-1.

The program counter holds the address of the next instruction to be executed. When the external reset is asserted, the program counter is loaded with 0, indicating that the bottom of memory holds the next instruction that will be fetched. Under the action of the clock, for single-cycle instructions, the instruction at the address in the program counter is loaded into the instruction register and the program counter is incremented. An instruction decoder determines the resulting action on the datapaths and the ALU. A long instruction is held in 2 bytes and an additional clock cycle is

TABLE 7-1 Instruction set for the *RISC_SPM* machine.

Instr	Instruction Word			Action
	opcode	src	dest	
NOP	0000	??	??	none
ADD	0001	src	dest	$\text{dest} \leq \text{src} + \text{dest}$
SUB	0010	src	dest	$\text{dest} \leq \text{dest} - \text{src}$
AND	0011	src	dest	$\text{dest} \leq \text{src} \& \text{dest}$
NOT	0100	src	dest	$\text{dest} \leq \sim \text{src}$
RD*	0101	??	dest	$\text{dest} \leq \text{memory}[\text{Add_R}]$
WR*	0110	src	??	$\text{memory}[\text{Add_R}] \leq \text{src}$
BR*	0111	??	??	$\text{PC} \leq \text{memory}[\text{Add_R}]$
BRZ*	1000	??	??	$\text{PC} \leq \text{memory}[\text{Add_R}]$
HALT	1111	??	??	Halts execution until reset

*Requires a second word of data; ? denotes a don't-care.

required to execute the instruction. In the second cycle of execution, the second byte is fetched from memory at the address held in the program counter and then the instruction is completed. Intermediate contents of the ALU may be meaningless when two-cycle operations are being executed.

7.3.5 RISC SPM: Controller Design

The machine's controller will be designed as an FSM. Its states must be specified, given the architecture, instruction set, and clocking scheme used in the design. This can be accomplished by identifying what steps must occur to execute each instruction. We will use an ASM chart to describe the activity within the machine, *RISC_SPM*, and to present a clear picture of how the machine operates under the command of its instructions.

The machine has three phases of operation: *fetch*, *decode*, and *execute*. Fetching retrieves an instruction from memory, decoding decodes the instruction, manipulates datapaths, and loads registers; execution generates the results of the instruction. The fetch phase will require two clock cycles—one to load the address register and one to retrieve the addressed word from memory. The decode phase is accomplished in one cycle. The execution phase may require zero, one, or two more cycles, depending on the instruction. The *NOT* instruction can execute in the same cycle that the instruction is decoded; single-byte instructions, such as *ADD*, take one cycle to execute, during which the results of the operation are loaded into the destination register. The source register can be loaded during the decode phase. The execution phase of a 2-byte instruction will take two cycles (e.g., *RD*)—one to load the address register with the

second byte and one to retrieve the word from the memory location addressed by the second byte and load it into the destination register. The controller for *RISC_SPM* has the 11 states listed below, with the control actions that must occur in each state.

<i>S_idle</i>	State entered after reset is asserted. No action.
<i>S_fet1</i>	Load the address register with the contents of the program counter. (Note: <i>PC</i> is initialized to the starting address by the reset action.) The state is entered at the first active clock after reset is de-asserted, and is revisited after a <i>NOP</i> instruction is decoded.
<i>S_fet2</i>	Load the instruction register with the word addressed by the address register and increment the program counter to point to the next location in memory, in anticipation of the next instruction or data fetch.
<i>S_dec</i>	Decode the instruction register and assert signals to control datapaths and register transfers.
<i>S_ex1</i>	Execute the <i>ALU</i> operation for a single-byte instruction, conditionally assert the zero flag, and load the destination register.
<i>S_rdl</i>	Load the address register with the second byte of a <i>RD</i> instruction, and increment the <i>PC</i> .
<i>S_rdl2</i>	Load the destination register with the memory word addressed by the byte loaded in <i>S_rdl</i> .
<i>S_wrl</i>	Load the address register with the second byte of a <i>WR</i> instruction, and increment the <i>PC</i> .
<i>S_wrl2</i>	Write the data stored in the source register filed of the instruction register to the memory location loaded in the address register in <i>S_wrl</i> .
<i>S_br1</i>	Load the address register with the second byte of a <i>BR</i> instruction, and increment the <i>PC</i> .
<i>S_br2</i>	Load the program counter with the memory word addressed by the byte loaded in <i>S_br1</i> .
<i>S_halt</i>	Default state to trap failure to decode a valid instruction.

The partitioned ASM chart for the controller of *RISC_SPM* is shown in Figure 7-12, with the states numbered for clarity. Once the ASM charts have been built, the designer can write the Verilog description of the entire machine, for the given architectural partition. This process unfolds in stages. First, the functional units are declared according to the partition of the machine. Then their ports and variables are declared and checked for syntax. Then the individual units are described, debugged, and verified. The last step is to integrate the design and verify that it has correct functionality.

The top-level Verilog module *RISC_SPM* integrates the modules of the architecture of Figure 7-10 and will be presented first. Three modules are instantiated: *Processing_Unit*, *Control_Unit*, and *Memory_Unit*, with instance names *M0_Processor*, *M1_Controller*, and *M2_Mem*, respectively. The parameters declared at this level of the hierarchy size the datapaths between the three structural/functional units.

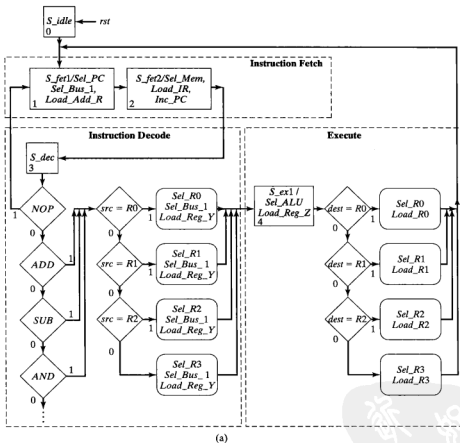


FIGURE 7-12 ASM charts for the controller of a processor that implements the RISC_SPM instruction set: (a) NOP, ADD, SUB, AND, (b) RD, (c) WR, (d) NOT, and (e) BR, BRZ.

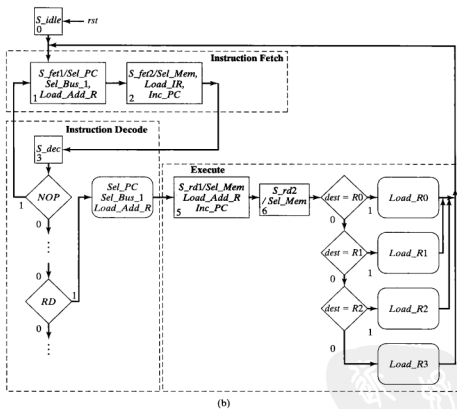


FIGURE 7-12 Continued

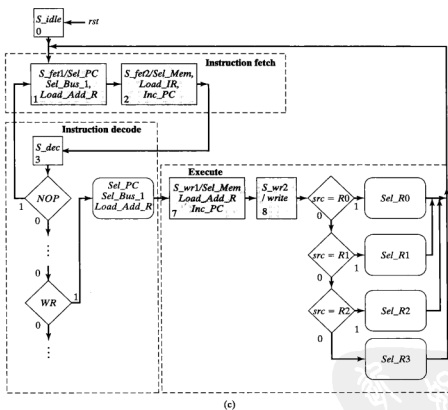


FIGURE 7-12 Continued

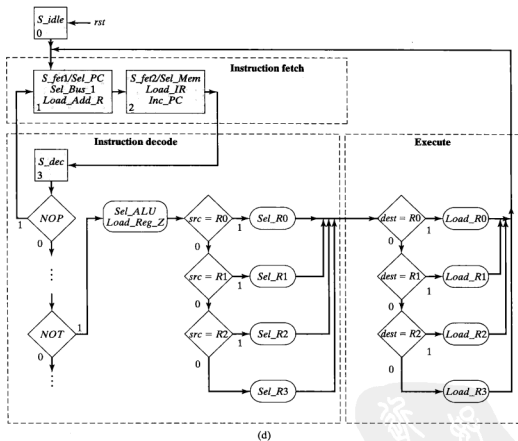


FIGURE 7-12 Continued

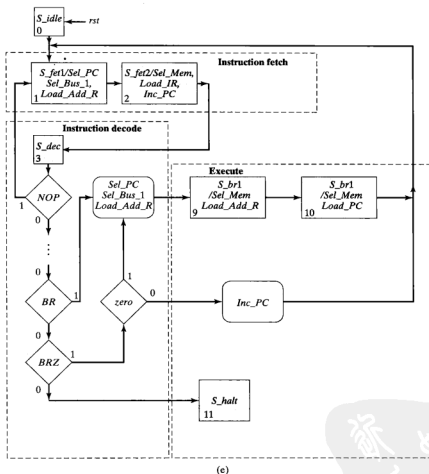


FIGURE 7-12 Continued

```

module RISC_SPM #(parameter word_size = 8, Sel1_size = 3, Sel2_size = 2)(
  input clk, rst
);

  // Data Nets
  wire [Sel1_size -1: 0] Sel_Bus_1_Mux;
  wire [Sel2_size -1: 0] Sel_Bus_2_Mux;
  wire zero;
  wire [word_size -1: 0] instruction, address, Bus_1, mem_word;

  // Control Nets
  wire Load_R0, Load_R1, Load_R2, Load_R3, Load_PC, Inc_PC; Load_IR,
    Load_Add_R, Load_Reg_Y, Load_Reg_Z, write;

  Processing_Unit M0_Processor (instruction, address, Bus_1, zero, mem_word,
    Load_R0, Load_R1, Load_R2, Load_R3, Load_PC, Inc_PC, Sel_Bus_1_Mux,
    Sel_Bus_2_Mux, Load_IR, Load_Add_R, Load_Reg_Y, Load_Reg_Z, clk, rst);

  Control_Unit M1_Controller (Sel_Bus_2_Mux, Sel_Bus_1_Mux, Load_R0,
    Load_R1, Load_R2, Load_R3, Load_PC, Inc_PC, Load_IR, Load_Add_R,
    Load_Reg_Y, Load_Reg_Z, write, instruction, zero, clk, rst);

  Memory_Unit M2_MEM (
    .data_out(mem_word),
    .data_in(Bus_1),
    .address(address),
    .clk(clk),
    .write(write) );
endmodule

```

The Verilog model of the machine's processor will describe the architecture, register operations, and datapath operations that are represented by the functional units shown in Figure 7-10. The processor instantiates several other modules, which must be declared too.

```

module Processing_Unit #(parameter
  word_size = 8, op_size = 4, Sel1_size = 3, Sel2_size = 2)(
  output [word_size -1: 0] instruction, address, Bus_1,
  output Zflag,
  input [word_size -1: 0] mem_word,
  input Load_R0, Load_R1, Load_R2, Load_R3, Load_PC,
    Inc_PC,
  input [Sel1_size -1: 0] Sel_Bus_1_Mux,
  input [Sel2_size -1: 0] Sel_Bus_2_Mux,
  input Load_IR, Load_Add_R, Load_Reg_Y, Load_Reg_Z,
  input clk, rst
);

  wire [word_size -1: 0] Bus_2;
  wire [word_size -1: 0] R0_out, R1_out, R2_out, R3_out;

```

```

wire [word_size -1: 0] PC_count, Y_value, alu_out;
wire alu_zero_flag;
wire [op_size -1 : 0] opcode = instruction [word_size-1: word_size-op_size];

Register_Unit R0 (R0_out, Bus_2, Load_R0, clk, rst);
Register_Unit R1 (R1_out, Bus_2, Load_R1, clk, rst);
Register_Unit R2 (R2_out, Bus_2, Load_R2, clk, rst);
Register_Unit R3 (R3_out, Bus_2, Load_R3, clk, rst);
Register_Unit Reg_Y (Y_value, Bus_2, Load_Reg_Y, clk, rst);
D_flop Reg_Z (Zflag, alu_zero_flag, Load_Reg_Z,
clk, rst);

Address_Register Add_R (address, Bus_2, Load_Add_R, clk, rst);
Instruction_Register IR (instruction, Bus_2, Load_IR, clk, rst);
Program_Counter PC (PC_count, Bus_2, Load_PC, Inc_PC,
clk, rst);

Multiplexer_5ch Mux_1 (Bus_1, R0_out, R1_out, R2_out,
R3_out, PC_count,
Sel_Bus_1_Mux);

Multiplexer_3ch Mux_2 (Bus_2, alu_out, Bus_1, mem_word,
Sel_Bus_2_Mux);

Alu_RISC ALU (alu_out, alu_zero_flag, Y_value, Bus_1,
opcode);

endmodule

module Register_Unit #(parameter word_size = 8) (
output reg [word_size-1: 0] data_out,
input [word_size -1: 0] data_in,
input load, clk, rst
);
always @ (posedge clk, negedge rst)
if (rst == 1'b0) data_out <= 0; else if (load) data_out <= data_in;
endmodule

module D_flop (output reg data_out, input data_in, load, clk, rst);
always @ (posedge clk, negedge rst)
if (rst == 1'b0) data_out <= 0; else if (load == 1'b1) data_out <= data_in;
endmodule

module Address_Register #(parameter word_size = 8)(
output reg [word_size -1: 0] data_out,
input [word_size -1: 0] data_in,
input load, clk, rst
);
always @ (posedge clk, negedge rst)
if (rst == 1'b0) data_out <= 0; else if (load == 1'b1) data_out <= data_in;
endmodule

module Instruction_Register #(parameter word_size = 8)(
output reg [word_size -1: 0] data_out,
input [word_size -1: 0] data_in,
input load, clk, rst

```

```

);
always @ (posedge clk, negedge rst)
  if (rst == 1'b0) data_out <= 0; else if (load == 1'b1) data_out <= data_in;
endmodule

module Program_Counter #(parameter word_size = 8)(
  output reg [word_size-1: 0] count,
  input [word_size-1: 0] data_in,
  input Load_PC, Inc_PC,
  input clk, rst
);

always @ (posedge clk, negedge rst)
  if (rst == 1'b0) count <= 0;
  else if (Load_PC == 1'b1) count <= data_in;
  else if (Inc_PC == 1'b1) count <= count + 1;
endmodule

module Multiplexer_5ch #(parameter word_size = 8)(
  output [word_size-1: 0] mux_out,
  input [word_size-1: 0] data_a, data_b, data_c, data_d, data_e,
  input [2: 0] sel
);
assign mux_out = (sel == 0) ? data_a: (sel == 1)
                  ? data_b : (sel == 2)
                  ? data_c: (sel == 3)
                  ? data_d : (sel == 4)
                  ? data_e : 'bx;
endmodule

module Multiplexer_3ch #(parameter word_size = 8)(
  output [word_size-1: 0] mux_out,
  input [word_size-1: 0] data_a, data_b, data_c,
  input [1: 0] sel
);
assign mux_out = (sel == 0) ? data_a: (sel == 1) ? data_b : (sel == 2) ? data_c: 'bx;
endmodule

```

The ALU is modeled as combinational logic described by a level-sensitive cyclic behavior that is activated whenever the datapaths or the select bus changes. Parameters are used to make the description more readable and to reduce the likelihood of a coding error.

/*ALU Instruction	Action
ADD	Adds the datapaths to form data_1 + data_2.
SUB	Subtracts the datapaths to form data_1 - data_2.
AND	Takes the bitwise-and of the datapaths, data_1 & data_2.
NOT	Takes the bitwise Boolean complement of data_1.
*/	
// Note: the carries are ignored in this model.	

```

module Alu_RISC #(parameter word_size = 8, op_size = 4,
// Opcodes
NOP   = 4'b0000,
ADD   = 4'b0001,
SUB   = 4'b0010,
AND   = 4'b0011,
NOT   = 4'b0100,
RD    = 4'b0101,
WR    = 4'b0110,
BR    = 4'b0111,
BRZ   = 4'b1000
)
output reg [word_size-1: 0] alu_out,
output alu_zero_flag,
input [word_size-1: 0] data_1, data_2,
input [op_size-1: 0] sel
);
assign alu_zero_flag = ~|alu_out;
always@ (sel, data_1, data_2)
case (sel)
  NOP: alu_out = 0;
  ADD: alu_out = data_1 + data_2; // Reg_Y + Bus_1
  SUB: alu_out = data_2 - data_1;
  AND: alu_out = data_1 & data_2;
  NOT: alu_out = ~ data_2; // Gets data from Bus_1
  default: alu_out = 0;
endcase
endmodule

```

The control unit is rather large, but its design has a simple form, and its development follows directly from the ASM charts in Figure 7-12. First, declarations are made for the ports and variables needed to support the description. Then the datapath multiplexers are described with nested continuous assignments using the conditional (?...:) operator. Two cyclic behaviors are used: a level-sensitive behavior describes the combinational logic of the outputs and the next state, and an edge-sensitive behavior synchronizes the clock transitions.

```

module Control_Unit #(parameter
word_size = 8, op_size = 4, state_size = 4,
src_size = 2, dest_size = 2, Sel1_size = 3, Sel2_size = 2){
output [Sel2_size-1: 0] Sel_Bus_2_Mux,
output [Sel1_size-1: 0] Sel_Bus_1_Mux,
output reg Load_R0, Load_R1, Load_R2, Load_R3, Load_PC, Inc_PC,
Load_IR, Load_Add_R, Load_Reg_Y, Load_Reg_Z, write,
input [word_size-1: 0] instruction,
input zero, clk, rst
);

// State Codes
parameter S_idle = 0, S_fet1 = 1, S_fet2 = 2, S_dec = 3,

```



```

        S_ex1 = 4, S_rd1 = 5, S_rd2 = 6,
        S_wr1 = 7, S_wr2 = 8, S_br1 = 9, S_br2 = 10, S_halt = 11;

// Opcodes
parameter NOP = 0, ADD = 1, SUB = 2, AND = 3, NOT = 4, RD = 5, WR = 6,
        BR = 7, BRZ = 8;

// Source and Destination Codes
parameter R0 = 0, R1 = 1, R2 = 2, R3 = 3;

reg [state_size-1: 0] state, next_state;
reg Sel_ALU, Sel_Bus_1, Sel_Mem;
reg Sel_R0, Sel_R1, Sel_R2, Sel_R3, Sel_PC;
reg err_flag;
wire [op_size-1: 0] opcode = instruction[word_size-1: word_size - op_size];
wire [src_size-1: 0] src = instruction[src_size + dest_size-1: dest_size];
wire [dest_size-1: 0] dest = instruction[dest_size-1: 0];

// Mux selectors
assign Sel_Bus_1_Mux[Sel1_size-1: 0] = Sel_R0 ? 0:
        Sel_R1 ? 1:
        Sel_R2 ? 2:
        Sel_R3 ? 3:
        Sel_PC ? 4: 3'bx; // 3-bits, sized number

assign Sel_Bus_2_Mux[Sel2_size-1: 0] = Sel_ALU ? 0:
        Sel_Bus_1 ? 1:
        Sel_Mem ? 2: 2'bx;

always @ (posedge clk, negedge rst) begin: State_transitions
    if (rst == 0) state <= S_idle; else state <= next_state; end

/* always @ (state, instruction, zero) begin: Output_and_next_state
Note: The above sensitivity list leads to incorrect operation. The state transition causes
the activity to be evaluated once, then the resulting instruction change causes it to be
evaluated again, but with the residual value of opcode. On the second pass the value
seen is the value opcode had before the state change, which results in Sel_PC = 0 in
state 3, which will cause a return to state 1 at the next clock. Finally, opcode is changed,
but this does not trigger a re-evaluation because it is not in the event control expression.
So, the caution is to be sure to use opcode in the sensitivity list. That way, the final execution
of the behavior uses the value of opcode that results from the state change, and
leads to the correct value of Sel_PC.
*/

always @ (state, opcode, src, dest, zero) begin: Output_and_next-state
    Sel_R0 = 0; Sel_R1 = 0; Sel_R2 = 0; Sel_R3 = 0; Sel_PC = 0;
    Load_R0 = 0; Load_R1 = 0; Load_R2 = 0; Load_R3 = 0; Load_PC = 0;
    Load_IR = 0; Load_Add_R = 0; Load_Reg_Y = 0; Load_Reg_Z = 0;
    Inc_PC = 0;
    Sel_Bus_1 = 0;
    Sel_ALU = 0;
    Sel_Mem = 0;
    write = 0;
    err_flag = 0; // Used for de-bug in simulation

```

```

next_state = state;
case (state)
  S_idle:
    S_fet1:
      next_state = S_fet1;
      begin
        next_state = S_fet2;
        Sel_PC = 1;
        Sel_Bus_1 = 1;
        Load_Add_R = 1;
      end
    S_fet2:
      begin
        next_state = S_dec;
        Sel_Mem = 1;
        Load_IR = 1;
        Inc_PC = 1;
      end
    S_dec:
      case (opcode)
        NOP: next_state = S_fet1;
        ADD, SUB, AND: begin
          next_state = S_ex1;
          Sel_Bus_1 = 1;
          Load_Reg_Y = 1;
          case (src)
            R0: Sel_R0 = 1;
            R1: Sel_R1 = 1;
            R2: Sel_R2 = 1;
            R3: Sel_R3 = 1;
            default err_flag = 1;
          endcase
        end // ADD, SUB, AND
        NOT: begin
          next_state = S_fet1;
          Load_Reg_Z = 1;
          Sel_ALU = 1;
          case (src)
            R0: Sel_R0 = 1;
            R1: Sel_R1 = 1;
            R2: Sel_R2 = 1;
            R3: Sel_R3 = 1;
            default err_flag = 1;
          endcase
        case (dest)
          R0: Load_R0 = 1;
          R1: Load_R1 = 1;
          R2: Load_R2 = 1;
          R3: Load_R3 = 1;
          default err_flag = 1;
        endcase
      end // NOT
      RD: begin
        next_state = S_rd1;
        Sel_PC = 1; Sel_Bus_1 = 1; Load_Add_R = 1;
      end

```

```

end // RD
WR: begin
    next_state = S_wr1;
    Sel_PC = 1; Sel_Bus_1 = 1; Load_Add_R = 1;
end // WR
BR: begin
    next_state = S_br1;
    Sel_PC = 1; Sel_Bus_1 = 1; Load_Add_R = 1;
end // BR
BRZ: if (zero == 1) begin
    next_state = S_br1;
    Sel_PC = 1; Sel_Bus_1 = 1; Load_Add_R = 1;
end // BRZ
else begin
    next_state = S_fet1;
    Inc_PC = 1;
end
default: next_state = S_halt;
endcase // (opcode)

S_ex1: begin
    next_state = S_fet1;
    Load_Reg_Z = 1;
    Sel_ALU = 1;
    case (dest)
        R0: begin Sel_R0 = 1; Load_R0 = 1; end
        R1: begin Sel_R1 = 1; Load_R1 = 1; end
        R2: begin Sel_R2 = 1; Load_R2 = 1; end
        R3: begin Sel_R3 = 1; Load_R3 = 1; end
        default: err_flag = 1;
    endcase
end

S_rd1: begin
    next_state = S_rd2;
    Sel_Mem = 1;
    Load_Add_R = 1;
    Inc_PC = 1;
end

S_wr1: begin
    next_state = S_wr2;
    Sel_Mem = 1;
    Load_Add_R = 1;
    Inc_PC = 1;
end

S_rd2: begin
    next_state = S_fet1;
    Sel_Mem = 1;
    case (dest)
        R0: Load_R0 = 1;
        R1: Load_R1 = 1;
        R2: Load_R2 = 1;
    end
end

```

```

                                R3:      Load_R3 = 1;
                                default    err_flag = 1;
                                endcase
                                end
S_wr2:      begin
                                next_state = S_fet1;
                                write = 1;
                                case (src)
                                    R0:      Sel_R0 = 1;
                                    R1:      Sel_R1 = 1;
                                    R2:      Sel_R2 = 1;
                                    R3:      Sel_R3 = 1;
                                    default    err_flag = 1;
                                endcase
                                end
S_br1:      begin next_state = S_br2; Sel_Mem = 1;
                                Load_Add_R = 1; end
S_br2:      begin next_state = S_fet1; Sel_Mem = 1;
                                Load_PC = 1; end
S_halt:     next_state = S_halt;
default:    next_state = S_idle;

                                endcase
                                end
                                endmodule

```

For simplicity, the memory unit of the machine is modeled as an array of D-type flip-flops. An alternative would be to use an external static RAM.

```

module Memory_Unit #(parameter word_size = 8, memory_size = 256)
output [word_size -1: 0] data_out,
input [word_size -1: 0] data_in,
input [word_size -1: 0] address,
input clk, write
);
reg [word_size -1: 0] memory [memory_size-1: 0];

assign data_out = memory[address];
always @ (posedge clk)
if (write) memory[address] <= data_in;
endmodule

```

7.3.6 RISC SPM: Program Execution

A testbench for verifying that *RISC_SPM* executes a stored program¹⁰ is given in page 374. *test_RISC_SPM* defines probes to display individual words in memory, uses a one-shot (*initial*) behavior to flush memory, and loads a small program and data into separate

¹⁰An assembler for the machine is located at the website for this book, and can be used to generate programs for use in embedded applications of the processor.

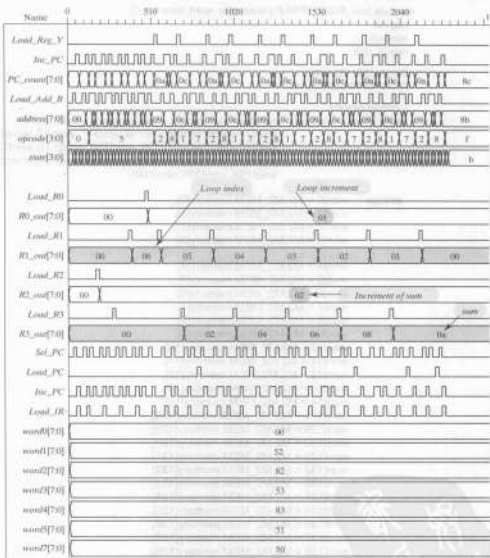


FIGURE 7-13 Simulation results produced by executing a stored program with RISC_SPM.

areas of memory. The program (1) reads memory and loads the data into the registers of the processor, (2) executes subtraction to decrement a loop counter, (3) adds register contents while executing the loop, and (4) branches to a halt when the loop index is 0. This sequence of instructions demonstrates the machine's ability to execute a "for" loop. The results of executing the program are displayed in Figure 7-13.

```

module test_RISC_SPM #(parameter word_size = 8)();
  reg rst;
  wire clk;
  reg [8:0] k;

  Clock_Unit M1 (clk);
  RISC_SPM M2 (clk, rst);

  // define probes
  wire [word_size-1:0] word0, word1, word2, word3, word4, word5, word6,
    word7, word8, word9, word10, word11, word12, word13,
    word14, word128, word129, word130, word131, word132,
    word133, word134, word135, word136, word137, word255,
    word138, word139, word140;

  assign word0 = M2.M2_MEM.memory[0],
    word1 = M2.M2_MEM.memory[1],
    word2 = M2.M2_MEM.memory[2],
    word3 = M2.M2_MEM.memory[3],

    word4 = M2.M2_MEM.memory[4],
    word5 = M2.M2_MEM.memory[5],
    word6 = M2.M2_MEM.memory[6],
    word7 = M2.M2_MEM.memory[7],
    word8 = M2.M2_MEM.memory[8],
    word9 = M2.M2_MEM.memory[9],
    word10 = M2.M2_MEM.memory[10],
    word11 = M2.M2_MEM.memory[11],
    word12 = M2.M2_MEM.memory[12],
    word13 = M2.M2_MEM.memory[13],
    word14 = M2.M2_MEM.memory[14],
    word128 = M2.M2_MEM.memory[128],
    word129 = M2.M2_MEM.memory[129],
    word130 = M2.M2_MEM.memory[130],
    word131 = M2.M2_MEM.memory[131],
    word132 = M2.M2_MEM.memory[132],
    word133 = M2.M2_MEM.memory[133],
    word134 = M2.M2_MEM.memory[134],
    word135 = M2.M2_MEM.memory[135],
    word136 = M2.M2_MEM.memory[136],
    word137 = M2.M2_MEM.memory[137],
    word138 = M2.M2_MEM.memory[138],
    word140 = M2.M2_MEM.memory[140],
    word255 = M2.M2_MEM.memory[255];

  initial #2800 $finish;

  // Flush Memory
  initial begin: Flush_Memory
    #2 rst = 0; for (k=0; k<=255; k=k+1) M2.M2_MEM.memory[k] = 0; #10 rst = 1;
  end

```

```

initial begin: Load_program
#5
M2.M2_MEM.memory[0] = 8'b0000_00_00; // opcode_src_dest
M2.M2_MEM.memory[1] = 8'b0101_00_10; // NOP
M2.M2_MEM.memory[2] = 130; // Read 130 to R2
M2.M2_MEM.memory[3] = 8'b0101_00_11; // Read 131 to R3
M2.M2_MEM.memory[4] = 131;
M2.M2_MEM.memory[5] = 8'b0101_00_01; // Read 128 to R1
M2.M2_MEM.memory[6] = 128;
M2.M2_MEM.memory[7] = 8'b0101_00_00; // Read 129 to R0
M2.M2_MEM.memory[8] = 129;
M2.M2_MEM.memory[9] = 8'b0010_00_01; // Sub R1-R0 to R1
M2.M2_MEM.memory[10] = 8'b1000_00_00; // BRZ
M2.M2_MEM.memory[11] = 134; // Holds address for BRZ
M2.M2_MEM.memory[12] = 8'b0001_10_11; // Add R2+R3 to R3
M2.M2_MEM.memory[13] = 8'b0111_00_11; // BR
M2.M2_MEM.memory[14] = 140;
// Load data
M2.M2_MEM.memory[128] = 6;
M2.M2_MEM.memory[129] = 1;
M2.M2_MEM.memory[130] = 2;
M2.M2_MEM.memory[131] = 0;
M2.M2_MEM.memory[134] = 139;
M2.M2_MEM.memory[139] = 8'b1111_00_00; // HALT
M2.M2_MEM.memory[140] = 9; // Recycle
end
endmodule

module Clock_Unit (output reg clock);
parameter delay = 0;
parameter half_cycle = 10;
initial begin #delay clock = 0; forever #half_cycle clock = ~clock; end
endmodule

```

7.4 Design Example: UART

Systems that exchange information and interact remotely via serial data channels use serializer/deserializer (SerDes) interfaces for conversion between serial and parallel formats of data.¹¹ There are many different architectures, coding schemes, and clocking schemes for such circuits. For simplicity, we will consider here a simple modem, which acts as an interface between a host machines/device and the serial data channel, as shown in Figure 7-14. A modem allows a computer to connect to a telephone line and communicate with a receiving computer [2, 5]. The host machine stores information in a parallel word format, but transmits and receives data in a serial, single-bit, format.

¹¹See, for example, reference material at National Semiconductor (www.national.com), or Google SerDes.